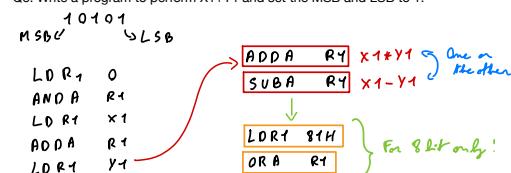


Q4. The question deals with a 4-bit programmable processor module. The function table of the ALU, and the instruction set of the processor are given in the Appendix.

Determine the contents of the Program Counter (PC), Accumulator (ACCA), and the Carry Bit (C) after the execution of each of the following instructions using the given initial values of the Input Switches (SW), Carry Bit (C), Program Counter (PC), Accumulator (ACCA) and content of the Memory Locations 2 (M2).


Q5. Write a program to perform $X_1 + Y_1$ and set the MSB and LSB to 1.




Half Adder :

x	y	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1



Full adder :

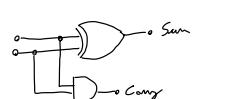


Cin	I1	S1	C1	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	1	0
1	0	1	1	0
1	1	0	1	1
1	1	1	1	1

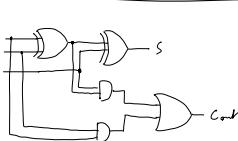

Multiplexer (Mux)

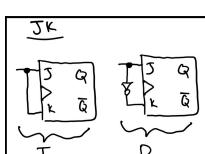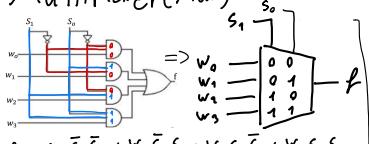

D - flip flop

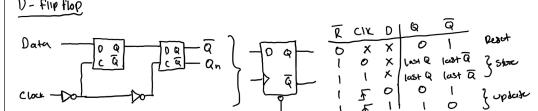

T - flip flop

